

Capacitors

$q(t) = Cv(t)$: charge across capacitor

$i = C \frac{dv}{dt}$ for constant C , current through capacitor

rewrite above to get $v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$

$P(t) = Cv(t) \cdot \frac{dv(t)}{dt}$: Power delivered to capacitors while charging

$w_c(t) = \frac{1}{2} Cv^2(t)$ J: Energy stored in a capacitor

$w_c(t) = \frac{1}{2C} q^2(t)$ J: Energy in terms of charge across plates

$C = \frac{\epsilon_0 A}{d}$: Capacitance formula

$\epsilon_0 = 8.85 \cdot 10^{-12} \text{F/m}$

Capacitors store energy in electric field, cannot provide more energy than amount stored within it

Voltage must be continuous, current can have discont.

Since current is dependent on dv/dt , blocks DC (open) at steady state, but will still store energy

Inductors

$\Phi(t) = Li(t)$: Magnetic flux created in an inductor

$L = \frac{v(t)}{\frac{di(t)}{dt}}$

$V(t) = L \frac{di(t)}{dt}$: Voltage from mag. field is proportional to r.o.c of current that created it

$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$: first term is about the history of the current, second is about the interval of interest

Inductors: voltage leads current, capacitors: current leads voltage

$P(t) = Li(t) \cdot \frac{di(t)}{dt}$

$w_L(t) = \frac{1}{2} Li^2(t)$: Energy stored in inductor

Current must be continuous, voltage can have discont.

Inductors short out DC (instead of opening) at steady state, but still store energy

First Order Circuits

Transient state & steady state, behaves like DC in steady state

Expo shape for V and I in transient, constant in steady

To solve:

- Find expression for voltage/current for transition period (while in transience)

- Find time constant τ defining how long circuit will be transient
- Find initial condition (for cap: $V_C(0-) = V_C(0+)$ for ind: $I_L(0-) = I_L(0+)$)
- Find steady state values
- This will require a first order DE

General form of solution: $\frac{dx(t)}{dt} + ax(t) = f(t)$

- $x(t)$: voltage or current
- $f(t)/A$: excitation, some voltage or current source
Sol. must be in form $x(t) = x_p(t) + x_c(t)$, x_p is particular solution, x_c is complementary solution
Start with constant excitation case, $f(t) = A$ where A is DC current/voltage.
This gives $x_p(t) = K_1 \frac{A}{a}$ with const. K_1
Complimentary solution is solution to homogenous equation
 $\frac{dx(t)}{dt} + ax(t) = 0$ (comp. solution is solution without external excitation and only internal conditions), leads to $x_c(t) = K_2 e^{-at}$ with some const. K_2
Therefore $x(t) = \frac{A}{a} + K_2 e^{-at}$, or $x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$
- Where $K_1/\frac{A}{a}$ is the steady-state solution, value of $x(t)$ when $t \rightarrow \infty$. Depends on excitation A
- K_1 is the steady state value, where $x(t)$ will settle. K_2 is difference between initial and steady-state value
- x_c is based on initial conditions
- τ is the time constant

At $t = \tau$, $x(t) = 0.368K_2$ (drops to 0.368 times initial value, assuming no excitation i.e $K_1 = 0$)

Mathematical Approach

- Use KVL/KCL to find expression for V/C somewhere in form
 $\frac{dx(t)}{dt} + ax(t) = A$
 - Use $i = C \frac{dv}{dt}$ or $L = \frac{v(t)}{\frac{di(t)}{dt}}$
- Try general solution $x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$
- Equate resulting constant/expo terms to find K_1, τ
- Find K_2 by using initial cond. $V_C(0-) = V_C(0+)/I_L(0-) = I_L(0+)$
- RC Circuit:
 $\tau = R_{Th}C$

$$i(t) = \frac{V_s}{R} e^{-\frac{t}{\tau}}$$

$$v(t) = V_s \left(1 - e^{-\frac{t}{\tau}}\right) \text{ where } V_s \text{ is steady state voltage}$$

RL Circuit:

$$\tau = \frac{L}{R_{Th}}$$

Steady state is $t > 5\tau$

Circuit Analysis Approach

- Assume solution in form $x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$
- Find either $V_C(0-)$ or $i_L(0-)$
 - Assuming circuit is at steady state before $t=0$
 - Capacitor \rightarrow open, inductor \rightarrow short, solve for value
- Find $x(0+)$
 - Replace capacitor with voltage source $V(0+)$, inductor $I(0+)$
- Find $x(\infty)$
 - Capacitor \rightarrow open, inductor \rightarrow short, solve $x(t)|_{t>5\tau}$
- Find τ
 - Form thevenin equiv. at terminals of storage element, then use $\tau = R_{Th}C$ or the L one
- Solve $K_1 = x(\infty)$, $K_2 = x(0+) - x(\infty)$

Second Order Circuits

Will be of form $\frac{d^2x}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2 x(t) = f(t)$

Solution will be of form $x(t) = x_p(t) + x_c(t)$, particular and complementary solution

x_p is with constant excitation, sol: $x_p(t) = \frac{A}{a_2}$

x_c is with no excitation. We assume solution $= e^{st}$ for const s , find first/second deriv, sub in, get characteristic eq $s^2 + a_1 s + a_2 = 0$

Solve quadratic eq $s = \frac{-a_1 \pm \sqrt{a_1^2 - 4a_2}}{2}$, if discriminant < 0 , let

$s = \alpha + j\omega$, $\alpha = -\frac{a_1}{2}$, $\omega = \frac{\sqrt{4a_2 - a_1^2}}{2}$, write solution as

$x_c(t) = C_1 e^{(a+j\omega)t} + C_2 e^{(a-j\omega)t}$, otherwise $x_c(t) = C_1 e^{s_1 t} + C_2 e^{s_2 t}$

Initially, will be overdamped (discriminant > 0)

Then we get two eqs $x(0) = K_1 + K_2$, $\left.\frac{dx(t)}{dt}\right|_{t=0} = K_1 s_1 + K_2 s_2$

How to solve

- Write the diff eq describing circuit for $t > 0$
- Find particular sol. $x_p(t) = \frac{A}{a_2}$
- Derive characteristic eq $s^2 + a_1s + a_2 = 0$ (note in physical terms $a_1 = 2\zeta\omega_0$ and $a_2 = \omega_0^2$)
- Quadratic formula
- 2 real unequal roots = overdamped, equal roots = critically damped, complex roots = underdamped
 - Overdamped: $x_c(t) = K_1e^{s_1t} + K_2e^{s_2t} = K_1e^{-(\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1})t} + K_2e^{-(\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1})t}$
 - Critically damped: $x_c(t) = B_1e^{-\zeta\omega_0t} + B_2te^{-\zeta\omega_0t}$ (where $s_1 = s_2 = -\zeta\omega_0$)
 - Underdamped: $x_c(t) = e^{-\zeta\omega_0t}[A_1\cos(\omega_0\sqrt{1 - \zeta^2}t) + A_2\sin(\omega_0\sqrt{1 - \zeta^2}t)]$
- $x(t) = x_p(t) + x_c(t)$, use initial conditions $(x(0), \frac{dx(0)}{dt})$ to find coefficients

Alternatively

- Use physical terms $a_1 = 2\zeta\omega_0$ and $a_2 = \omega_0^2$, match coefficients instead of characteristic eq, solve directly

$$-\frac{d^2x_c(t)}{dt^2} + 2\zeta\omega_0\frac{dx_c(t)}{dt} + \omega_0^2x_c(t) = 0$$

Note due to continuity of current/voltage we can replace inductors with current source $I = \text{steadystate}$ and V for capacitors only at $t = 0^+$

Complex Numbers

Complex numbers (rect): $z = a + jb$

Complex numbers (polar): $z = re^{j\theta}$, r is real axis and j is complex

Euler's identity: $e^{j\theta} = \cos(\theta) + j\sin\theta$, alternative complex notation

$$z = r\cos\theta + jr\sin\theta$$

$$\text{Rect} \rightarrow \text{polar}: r = \sqrt{a^2 + b^2}, \theta = \tan^{-1} \frac{b}{a}$$

$$\text{Polar} \rightarrow \text{rect}: a = r\cos\theta, b = r\sin\theta$$

$$\text{Complex conjugate of } a + jb : \bar{z} = a - jb, z\bar{z} = a^2 + b^2$$

Addition/subt: Just add/subtract componentwise

Multiplication:

$$z_1z_2 = \begin{cases} (a_1a_2 - b_1b_2) + j(a_1b_2 + a_2b_1) & \text{rect form} \\ r_1r_2e^{j(\theta_1+\theta_2)} & \text{polar form} \end{cases}$$

*note you should verify the polar angle is in the right quadrant

Division:

$$\frac{z_1}{z_2} = \begin{cases} \left(\frac{a_1 a_2 + b_1 b_2}{a_2^2 + b_2^2} \right) + j \left(\frac{b_1 a_2 - a_1 b_2}{a_2^2 + b_2^2} \right) & \text{rect form} \\ \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)} & \text{polar form} \end{cases}$$

Sinusoidal and Complex Forcing Functions

$x(t) = A \cos(\omega t + \theta)$, A is amplitude, ω angular frequency (rad/s), θ phase angle

$f = \frac{1}{T}$, f =frequency, T =period

$$\omega = 2\pi f = \frac{2\pi}{T}$$

any point on one waveform happens before another = leads, otherwise = lags

$$\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$$

$$\sin(\alpha - \beta) = \sin \alpha \cos \beta - \cos \alpha \sin \beta$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

$$\sin\left(\omega t + \frac{\pi}{2}\right) = \cos(\omega t)$$

$$\cos\left(\omega t - \frac{\pi}{2}\right) = \sin(\omega t)$$

$$\cos(\omega t \pm 180^\circ) = -\cos(\omega t)$$

$$\sin(\omega t \pm 180^\circ) = -\sin(\omega t)$$

To find phase diff:

- f must be the same
- A must be positive
- Both must be sin
- Then just find diff between their phase θ

If we introduce sinusoidal func into a linear network, other variables will become sinusoidal with same f

Euler's identity (adapted): $e^{j\omega t} = \cos \omega t + j \sin \omega t$

$x(t) = X_m e^{j(\omega t + \phi)} = X_m \cos(\omega t + \phi) + j X_m \sin(\omega t + \phi)$, X_m is maximum voltage/current (amplitude)

Put in your complex forcing function converted from sinusoidal, solve for a polar form complex number, then use Euler to get the $\text{Re}()$ part

Phasors

$$\tilde{V} = V_m e^{j\theta} \text{ (real part of } v(t)\text{)}$$

Can also be $\tilde{V} = V_m \angle \theta$ (we can do this because we only need magnitude & phase)

$x(t) = X_m e^{j\theta} [e^{j\omega t}] \rightarrow x(t) = \tilde{X} [e^{j\omega t}]$ Sub this into KCL/KVL (same as doing with

complex forcing func, $e^{j\omega t}$ optional)

Creates phasor eq, which is algebraic

Freq. domain is when there is no time term, only ω . Phasors transform time domain to freq. domain.

Phasor angles are based on cos, transform needed for sin

Time	Freq
$A \cos(\omega t \pm \theta)$	$A \angle (\pm \theta)$
$A \sin(\omega t \pm \theta)$	$A \angle (\pm \theta - 90^\circ)$

Solving

- Transform a set of diff. eqs in time domain to freq. domain
- Solve for all unknown phasors
- Transform phasors back

Resistor:

$$\tilde{V} = \tilde{I}R: V/I \text{ are in phase}$$

Inductor:

$$\tilde{V} = j\omega L \tilde{I} \text{ V/I are 90 deg out of phase (V leading)}$$

Capacitor:

$$\tilde{I} = j\omega C \tilde{V} \text{ V/I are 90 deg out of phase (I leading)}$$

$$\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} \text{ unit: ohms}$$

$$Z = |Z| \angle \theta_Z \text{ where } |Z| = \frac{V_m}{I_m}, \theta_Z = \theta_v - \theta_i$$

$$Z(\omega) = R(\omega) + jX(\omega), R(\omega) \text{ is resistive part, } X(\omega) \text{ is reactive part}$$

Resistor:

$$Z = R \text{ or } Z = R \angle 0^\circ$$

Inductor:

$$Z = j\omega L \text{ or } Z = \omega L \angle 90^\circ$$

Capacitor:

$$Z = \frac{1}{j\omega C} \text{ or } Z = \frac{1}{\omega C} \angle (-90^\circ) \text{ or } Z = -\frac{j}{\omega C}$$

$$\text{Series: } Z_0 + Z_1 + \cdots + Z_n = Z_{tot}$$

$$\text{Parallel: } \frac{1}{Z_0} + \frac{1}{Z_1} + \cdots + \frac{1}{Z_n} = \frac{1}{Z_{tot}}$$

Z is not a phasor, it represents only a complex number not a sinusoidal func

To Solve AC:

- Express $x(t)$ as a phasor

- Find impedance of each element
- Combine impedances, apply KVL/KCL to solve circuit
- Solve for \tilde{X}
- Convert back to $x(t)$

$$Y = \frac{1}{Z}$$

$$\tilde{Y} = \frac{\tilde{I}}{\tilde{V}} \text{ unit: siemens}$$

Same stuff as Z

Opposite rules for series/parallel combinations

Summary:

- AC circuits with sinusoidal forcing functions
 - Use complex numbers to simplify analysis
- AC circuits with sinusoidal forcing functions (go back up a level by taking the real part)
 - Use phasors to simplify analysis
- AC circuits represented by phasors (go back up a level by multiplying by $e^{j\omega t}$)

For simple AC circuits, (eg. first order), use:

- $\tilde{V} = Z\tilde{I}$
- Series/parallel impedance rules
- KCL/KVL
- Voltage/current division
- Anything else you would use for DC but in freq. domain

For more complex AC circuits (eg. multiple sources), use:

- Nodal analysis
- Loop/mesh analysis
- Superposition
- Source transformation
- Thevenin/Norton's theorem